

1.

```
library IEEE;
```

```
use IEEE.std_logic_1164.all;
```

```
entity ent is
```

```
port(
```

```
    a: in std_logic;
```

```
    b: in std_logic;
```

```
    c: in std_logic;
```

```
    d: in std_logic;
```

```
    s1: out std_logic;
```

```
    s2: out std_logic;
```

```
    s3: out std_logic;
```

```
    s4: out std_logic
```

```
);
```

```
end ent;
```

```
architecture arc of ent is
```

```
begin
```

```
    process(a , b , c , d) is
```

```
    begin
```

```
        s1 <= a or (not b);
```

```
        s2 <= (a or (not b)) and c or d;
```


```
        s3 <= (a or (not b)) and (c or d);
```

```
        s4 <= (a or (not b)) and not(c or (a and d));
```

```
    end process;
```

```
end arc;
```

2.

 

3.

```
library IEEE;
```

```
use IEEE.std_logic_1164.all;
```

```
entity ent is
```

```
port(
```

```
    a: in bit_vector;
```

```
    b: in bit_vector;
```

```
    c: in bit_vector
```


```
);
```

```
end ent;
```

```
architecture arc of ent is
```

begin

4.

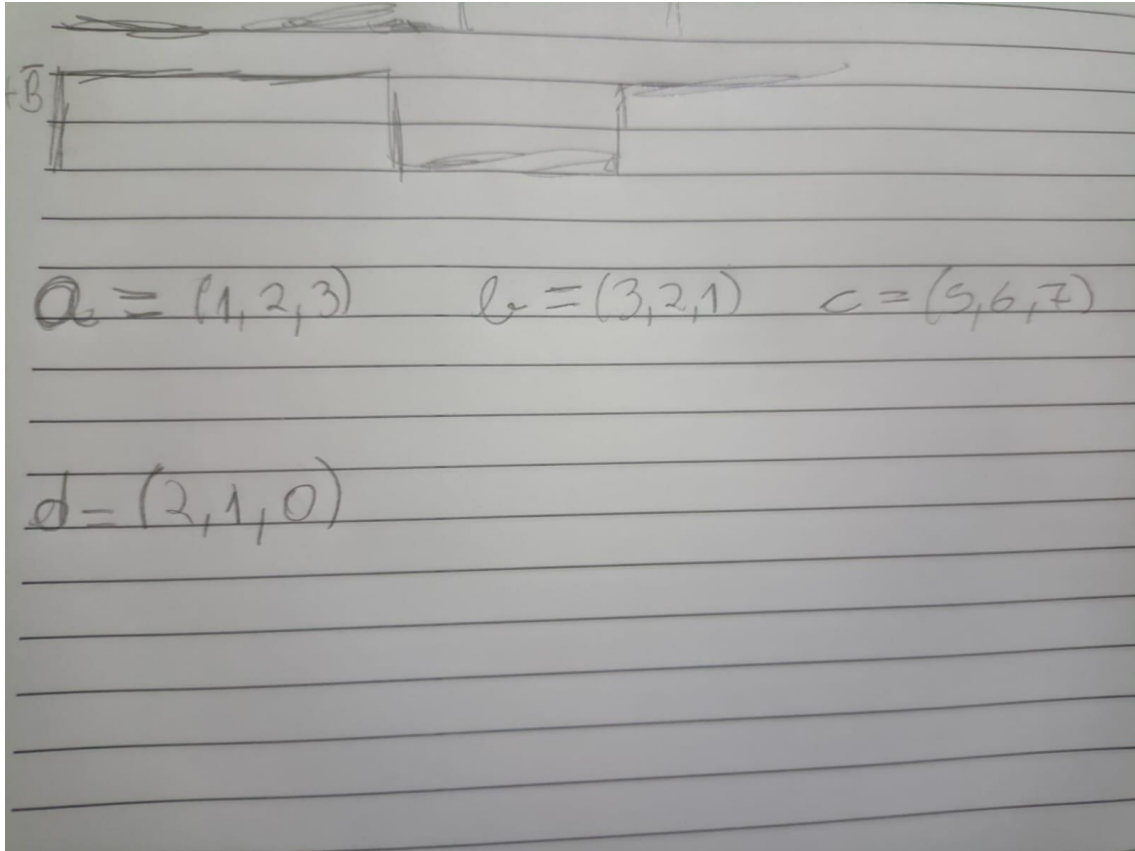

7. ENTITY corret_1 IScapa_1ra

PORT (a, b, c, d : IN BIT;

s : OUT BIT_VECTOR (5 DOWNT0 0));

END corret_1;

ARCHITECTURE teste OF corret_1 IS

BEGIN

s(0) <= (a AND b) OR (c AND d); -- opcao 1

--s(0) <= a AND (b OR c) AND d; -- opcao 2

s(1) <= (a NOR b) NOR c; -- opcao 1

--s(1) <= a NOR (b NOR c); -- opcao 2

```
s(2) <= (a AND b) OR c;    -- opcao 1
--s(2) <= a AND (b OR c);  -- opcao 2

s(3) <= NOT (a AND b) NAND c; -- correta
s(4) <= a XOR b XOR c;      -- correta
END teste;
```